



Hardware overview

HW1 will keep coming out

TA hours are on website

Moving my hours to Fridays at 11 (next week)




HW0 responses

Excited about: a lot!

Nervous about: low-level details, new course/workload, heard scary things about the topic, using the simulators

Helps your learning: in-class activities, having access to resources

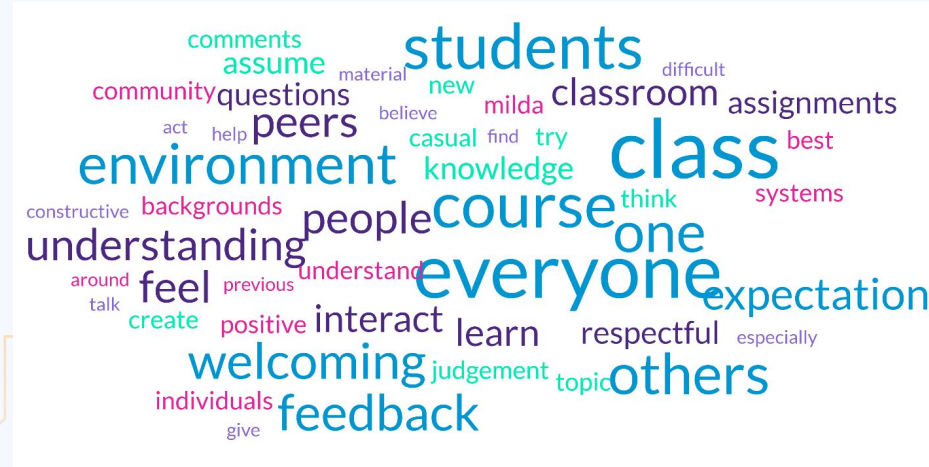Community: committed to welcoming environment + sustained communication! We want to focus on everyone's success and growth



source // another visualization // Babbage's analytical engine

???




Stored-program computers

Modern computers hinge on two principles:

- Instructions are represented in memory the same way as numbers
- Memory can be altered by programs

First principle means that:

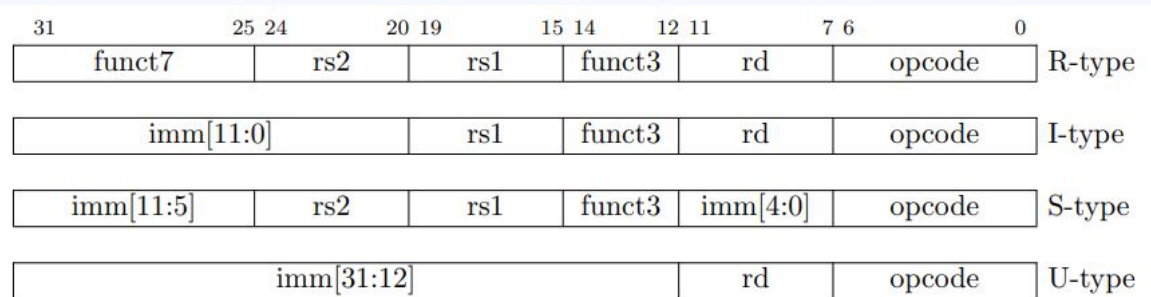- Instructions live in memory
- The CPU needs to have a way of interpreting an instruction, just as it would any other data in memory



HW assumptions we're working with

CPU can read bits from memory as electrical signals (one "wire" per bit)

Everything is a pure low/high signal, no noise/interference

For now, we're not worried about constraints (space, complexity, power)


Each "step" leaves enough time for circuit to stabilize

To run a program, CPU HW needs:

A way to extract/rearrange bits – pull out the relevant fields of an instruction

A way to implement combinational logic – arithmetic/logical, branching


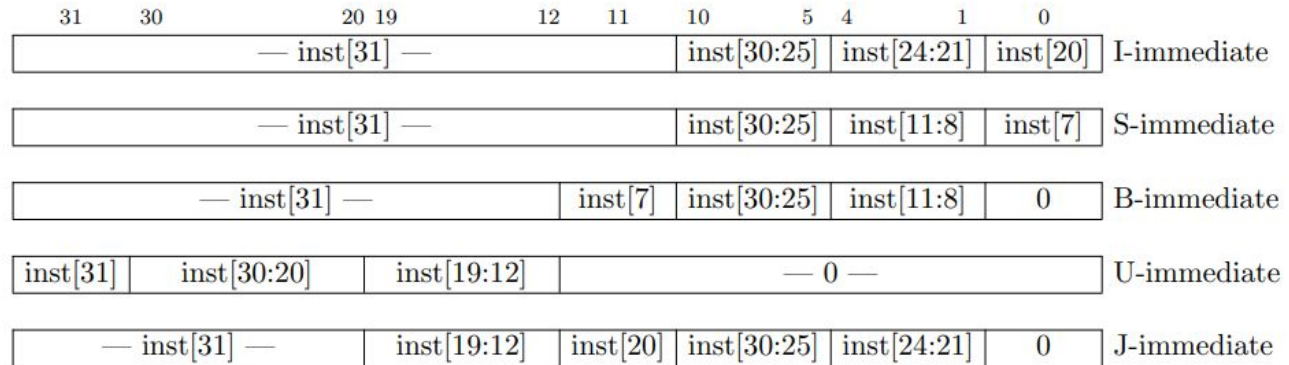
A way to keep track of state – what is the value of the PC at the current step?



Data as collections of wires

wire/data line: carries a single digital signal (on/off)

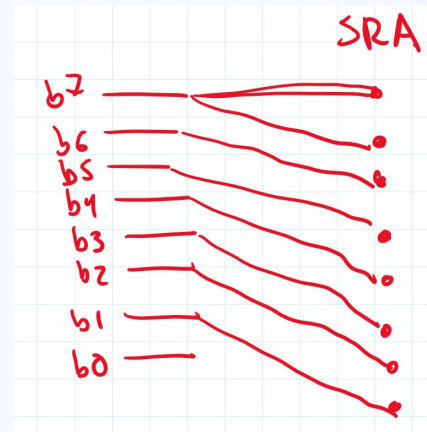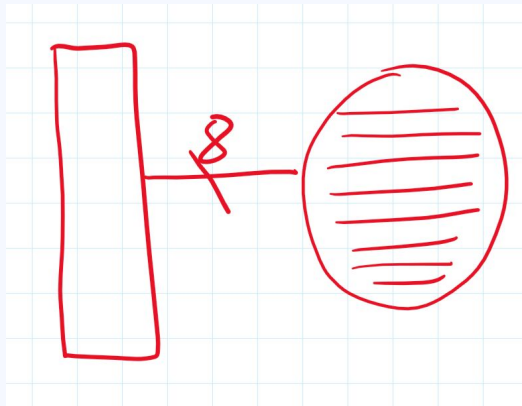bus (P&H definition): a collection of data lines that is treated as one, multi-bit signal



Combinational logic circuits


Examples: adders, logical operators, control signal translation

Work like pure functions (no memory)

Combinatorial expressions can be automatically synthesized to circuits



Physically, logic gates are implemented using transistors (electrical switches)

LOGIC GATE SYMBOLS

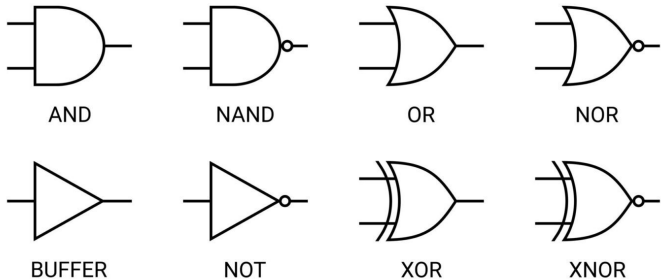

[image source](#)

“half adder” (sum and carry output):

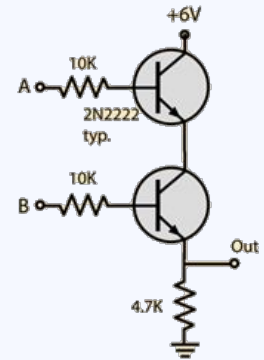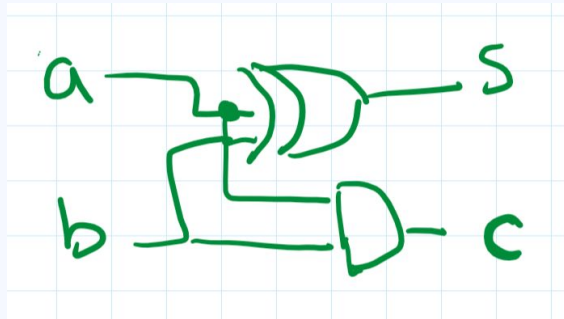




[image source](#)

Multiplexers

Used to select between multiple inputs

n-bit selector signal = select between 2^n inputs


Example: 2nd operand for add vs addi

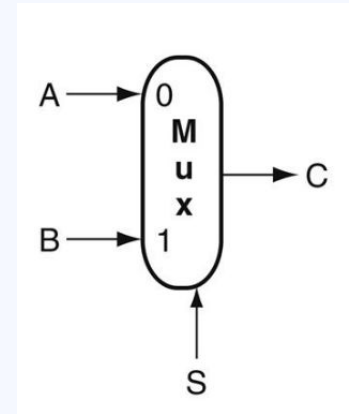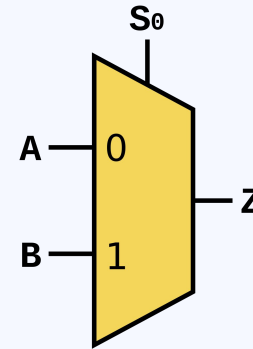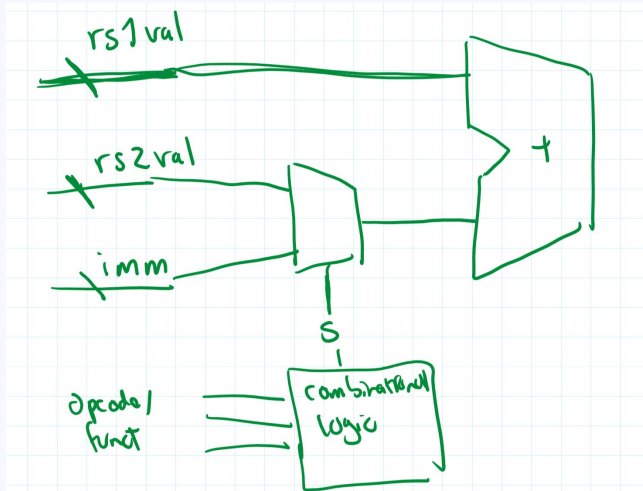


P&H Fig. A.3.2




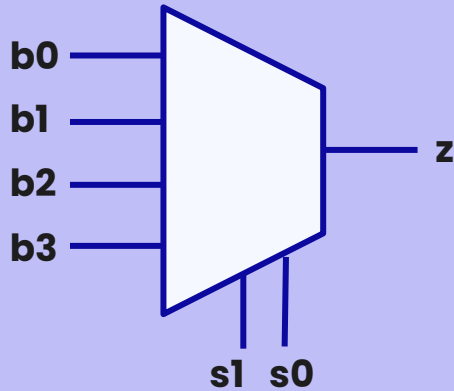Build a 4-input (2-bit selector) mux out of logic gates



LOGIC GATE SYMBOLS


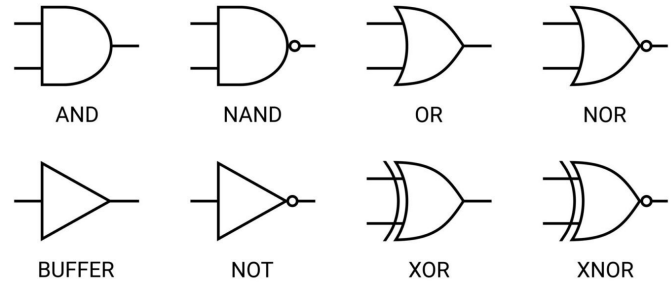


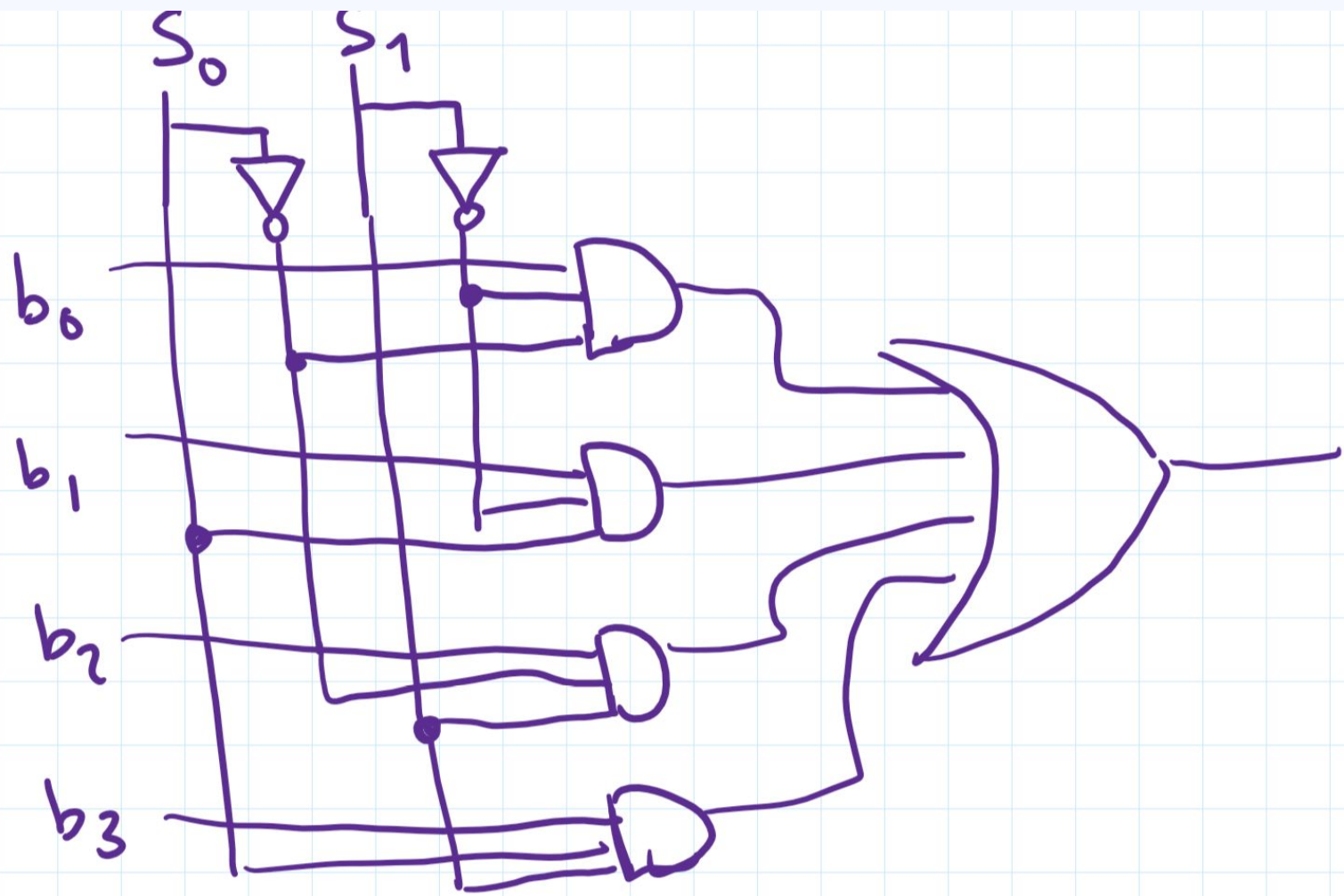

Arithmetic Logic Unit

“ALU”

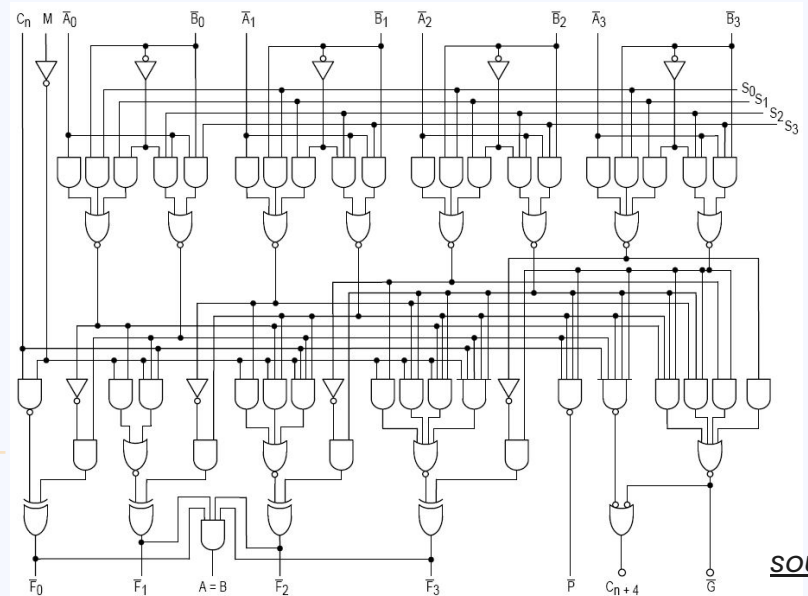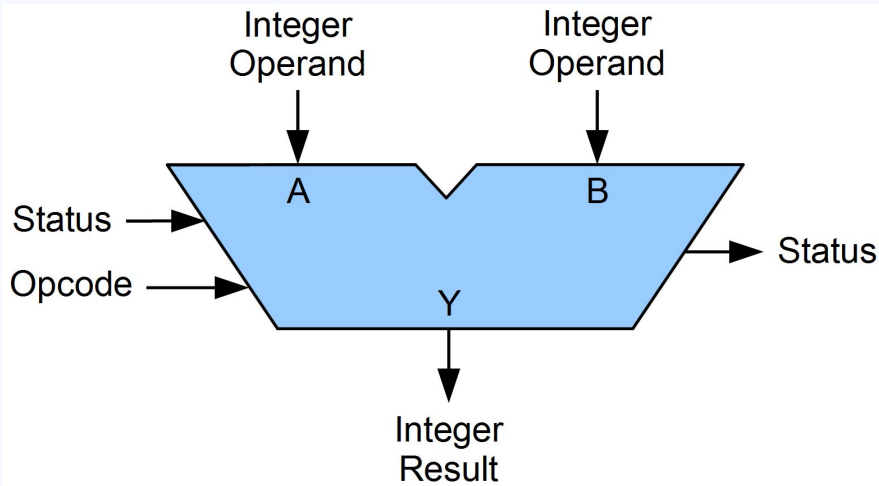Takes in two operands and a control signal for the operation, produces result of applying operation on operands (status input/output signals optional)



Components that have state


How do we express “at each step, increment the PC by 4?”

Need *clock signal* to control when state changes



Memory elements, such as flip flops and latches, have internal state that updates on clock tick (D flip-flop pictured)

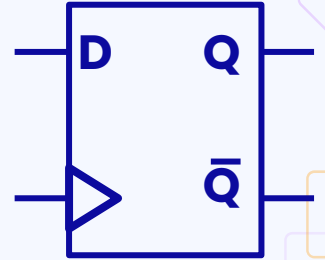Our abstraction of registers: each bit is stored in a D flip-flop





How do we express “at each clock tick,
increment the PC by 4” using a PC register and
an adder?

Takeaways

Bits of an instruction = electrical signals CPU uses to execute a program

CPU is just a (very, very) big circuit made up of wires, combinational logic elements, and memory elements

Can implement modules we need (multiplexers, ALUs, bit selectors, registers) using these elements

Basically: we have an “existence proof” of the hardware we need, so we can start working one level of abstraction higher to implement a CPU

Hardware description languages

Used to describe circuits (often for synthesis into a circuit, such as on an FPGA)

Examples: Verilog, VHDL

Defines behavior of combinational components and memory components

Updates in a block are done in *parallel* – Verilog example:

```
reg a, r;
always @(posedge clk) begin
    a <= ~r;
    r <= r + 1;
end
```

We won't be working in HDL – but a C++ approximation of it in simulation



Let's build a CPU!

What do we need to get started?

